



臺灣大學

# IC Design HW4 Tutorial

TA: Pi-Chuan Chen

Advisor: Tzi-Dar Chiueh

2023/11/30



臺灣大學

# Outline

- Workflow & Notification of HW4
- Standard Cell Library
- Tips
- Verification
- Reminder



臺灣大學

# Workflow (1/2)

- Grading

- Approximation error (35%)
- Performance (35%)
- Report (30%)

- First, design a circuit that can finish the simulation.

```
=====
Simulation finished
=====
```

- Second, decrease the CYCLE in tb.v until it fail (CYCLE < critical path). e.g some output values and corresponding MSE become x.



臺灣大學

## Workflow (2/2)

- Third, find the MSE and number of transistors in your design.

```
=====
                        Summary
=====
Clock cycle:                10.0 ns
Number of transistors:      1061
Total excution cycle:      256
Approximation Error Score: 17987801.0
Performance Score:          2716160.0
=====
```

- Finally, modify you design to achieve better accuracy and performance.
  - Trade-off between area & speed. e.g. Try different adders, carry-skip, carry-lookahead, etc.
  - Try different algorithms. e.g. try different number of segments, different points, different slopes.



臺灣大學

# Notification (1/2)

- In this HW, all the logic operations **MUST** consist of standard cells (defined in lib.v). You can **NOT** use logic operators.

~~wire a, b, c;  
assign a = b & c;~~

→ Behavioral Modeling

wire a, b, c;  
AN2 an(a, b, c);

→ Structural Modeling




臺灣大學
 
## Notification (2/2)

- Do NOT change any module name and port name in sigmoid.v, just modify the module description, otherwise you can't pass the simulation.

```
module sigmoid (  
    input        clk,  
    input        rst_n,  
    input        i_in_valid,  
    input  [ 7:0] i_x,  
    output [15:0] o_y,  
    output        o_out_valid,  
    output [50:0] number  
);
```



**Don't  
Change**

- Use FD2 (positive edge) module for flip flop.



臺灣大學

# Standard Cell Library



# Standard Cell Library (lib.v)

臺灣大學

- Choose what you need
- Compose your circuit according to I/O connections
- IV // not
- AN3
- AN4
- AN2
- EN // xnor
- EN3
- EO // xor
- EO3
- FA1 // full adder
- FD1 // negative edge DFF
- FD2 // positive edge DFF
- ND2 // nand
- ND3
- ND4
- NR2 // nor
- NR3
- OR2 // or
- OR3
- OR4
- HA1 // half adder
- MUX21H // 2-to-1 MUX





臺灣大學

# Number of Transistors

- “+” operator is only allowed to add up the transistor count of each cell.

```
module Reg3(  
    input        CLK,  
    input        RESET,  
    input  [ 2:0] DD,  
    output [ 2:0] Q,  
    output [50:0] Reg3_num  
);  
  
wire [50:0] FD_num0, FD_num1, FD_num2;  
assign Reg3_num = FD_num0 + FD_num1 + FD_num3;  
  
FD2 fd0(Q[0], DD[0], CLK, RESET, number);  
FD2 fd1(Q[1], DD[1], CLK, RESET, number);  
FD2 fd2(Q[2], DD[2], CLK, RESET, number);  
  
endmodule
```

```
module DUT (  
    input        clk,  
    input        rst_n,  
    input  [ 2:0] A,  
    input  [ 2:0] B,  
    output [ 2:0] C,  
    output [50:0] DUT_num  
);  
  
wire [50:0] num0, num1;  
assign DUT_num = num0 + num1;  
  
wire [2:0] A_reg, B_reg;  
Reg3 rr0(A_reg, A[2:0], clk, rst_n, num0);  
Reg3 rr0(B_reg, B[2:0], clk, rst_n, num1);  
  
endmodule
```



臺灣大學

# Tips



臺灣大學

# Parameterized module

- Verilog “generate” statement
  - Copy the codes.
  - Instantiate multiple modules easily.
- Use generate and parameter to define parameterized module.
  - High flexibility.
  - High readability.
  - Shorten your codes.
  - Prevent wire misconnection.

# Example - n-bit DFF

```
module REGP#(  
    parameter BW = 2  
)(  
    input      clk,  
    input      rst_n,  
    output [BW-1:0] Q,  
    input  [BW-1:0] D,  
    output [ 50:0] number  
)  
  
wire [50:0] numbers [0:BW-1];
```

```
genvar i;  
generate  
    for (i=0; i<BW; i=i+1) begin  
        FD2 f0(Q[i], D[i], clk, rst_n, numbers[i]);  
    end  
endgenerate
```



Generate FD2 according to BW.

```
//sum number of transistors  
reg [50:0] sum;
```

```
integer j;  
always @(*) begin  
    sum = 0;  
    for (j=0; j<BW; j=j+1) begin  
        sum = sum + numbers[j];  
    end  
end
```



Use for loop to sum transistor counts.

```
assign number = sum;
```

```
endmodule
```

Instantiate in top module.



```
REGP#(.BW(5)) U_REGP( .clk(clk), .rst_n(rst_n), .Q(q), .D(D), .number(number));
```



臺灣大學

# Verification




臺灣大學

# Test and Verify Your Circuit

- By applying input patterns and observing output responses

## Testbench

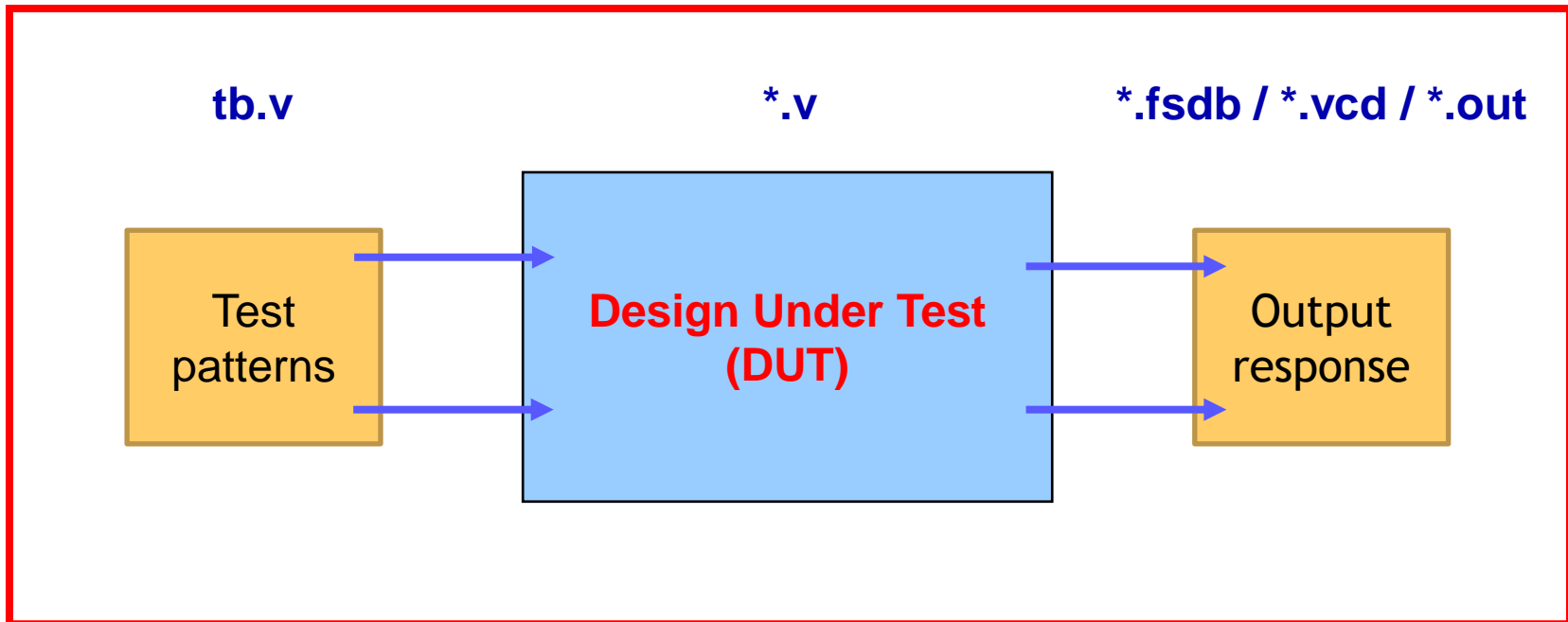



臺灣大學

# Compile and debug

- Source

- source /usr/cad/synopsys/CIC/vcs.cshrc

- Include the tb.v & lib.v files to run simulation

- vcs tb.v sigmoid.v lib.v -full64 -R -debug\_access+all +v2k
  - vcs tb.v sigmoid.v lib.v -full64 -R -debug\_access+all +v2k +define+DEBUG
  - vcs tb.v sigmoid.v lib.v -full64 -R -debug\_access+all +v2k +define+PIPELINE
  - vcs tb.v sigmoid.v lib.v -full64 -R -debug\_access+all +v2k +define+DEBUG+PIPELINE



臺灣大學

# Reminder (1/2)

- Loosen the clock cycle when you're checking your circuit logic.
- Once the logic is correct, start to shorten the clock period to find the critical path.
- Use basic gates provided in lib.v to design your circuit.  
**No behavior level code will be accepted.**





臺灣大學

## Reminder (2/2)

- Due on 2023/12/14 9:00
- For any further questions, contact TA.
  - r11943013@ntu.edu.tw
- To know more about Verilog, refer to
  - [http://www.ece.umd.edu/courses/enee359a.S2008/verilog\\_tutorial.pdf](http://www.ece.umd.edu/courses/enee359a.S2008/verilog_tutorial.pdf)