

IC Design

Homework # 4

Due 2023/12/14, 9:00, Verilog code and report upload to NTUCool, no hardcopy


Plagiarism is not allowed. 10% penalty for each day of delay.

Problem Specification

Design a circuit with reset that computes the **approximation of the sigmoid function**. There are two input signals for the circuit, i.e., i_x with 8 bits, and a 1-bit i_{in_valid} . The i_x is a fixed-point format with a 1-bit sign, 2-bit integer, and 5-bit fraction. The circuit contains two output signals, i.e., up to 16-bit o_y for the approximation output value, and a 1-bit o_{out_valid} . The o_y is a fixed-point format with 1-bit integer and up to 15-bit fraction, and you don't need to use all 15 bits for your design's output. Note that **the input signal is signed**, and **the output signal is unsigned**. The relation between the input and the output signals is


$$Y \cong \text{sigmoid}(x) = \frac{1}{1 + e^{-x}}$$

You are encouraged to use piecewise-linear approximation to design your circuit. For example, Figure 1 uses three segments to approximate the real function, while Figure 2 uses 5 segments. Figure 2 is more accurate than Figure 1, but its cost is using more transistors in the circuit because it needs to calculate more slopes. This is a tradeoff, so it is important to think about what your approximation function is before designing the circuit. Note that this homework only considers the range of $[-4, 4]$.

 


The following diagram illustrates the relation between your design and the testbench. Pull up “ o_{out_valid} ” and output your answer to “ $o_y[15:0]$ ” once your circuit

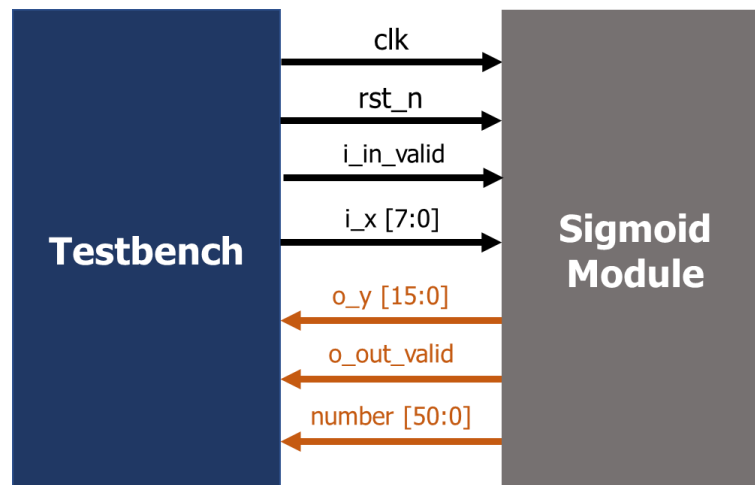finishes the calculation, the testbench will then check your answers. Note that the output signals: “o_y[15:0]” and “o_out_valid” must be registered, i.e., they are outputs of DFFs **(use module FD2 (positive edge) in lib.v)**.



Timing Diagram

 When your design is simulated in testbench, the circuit would only be reset once. After reset, **new values of i_x would be input at every cycle**. Besides, **o_out_valid should remain high once it is pulled up**, and the order of input i_x and their corresponding output o_y should not be changed **(First in, first out.)**.



Signals Description

Signal name	I/O	Width	Simple description
clk	Input	1	Clock signal.
rst_n	Input	1	Active low asynchronous reset.
i_in_valid	Input	1	Indicate that the input is valid.
i_x	Input	8	Input X.
o_y	Output	16	Approximate output Y. Up to 15 bits fraction.
o_out_valid	Output	1	Indicate that the calculation was finished.
number	Output	51	The number of transistors.

Design Rules

Those who do not design according to the following rules will not be graded.

- **LUT-based designs are not allowed.**
- There should be a **reset signal** for the register.
- You are free to add pipeline registers.
- You can loosen your simulation timing first, (i.e., ``define CYCLE XXXX` in the tb.v), then shorten the clock period to find your critical path.
- Your design should be based on the **standard cells in the lib.v**. All logic operations in your design **MUST consist of the standard cells** instead of using the operands such as “+”, “-”, “&”, “|”, “>”, and “<”.
- Using “assign” to concatenate signals or specify constant values is allowed.
- Design your homework in the given “sigmoid.v” file. **You are NOT ALLOWED to change the filename and the header of the top module (i.e. the module name and the I/O ports).**
- If your design contains more than one module, **don’t create a new file for them**, just put those modules in “sigmoid.v.”

Grading Policy

1. Gate-level design using Verilog (70%)

Your score will depend on both the approximation error and performance of your design.

(a) Approximation Error Score (35%)

At this stage, we will evaluate how much the value of the sigmoid module approximates the real one. Time and area are not considered. We provide a testbench with a total of 256 patterns, whose distribution is in [-4, 4), and 16-bit format. There will be a ranking according to mean square error (MSE):

$$\sum_{i=0}^{255} \frac{(Y_{\text{approximate},i} - Y_{\text{real},i})^2}{256}.$$

(b) Performance Score (35%)

At this stage, you need to **add up the number of transistors of all used cells in the div module and connect it to number [50:0]**.

Only in this section, you are allowed to use “+” to help with calculations.

```
assign number = gate_count[0] + gate_count[1] + gate_count[2] + gate_count[3];

DRIVER V1 (.A(pp_w[9]), .Z(pp1_W[10]), .number(gate_count[0]));
DRIVER V2 (.A(pp_w[9]), .Z(pp1_W[11]), .number(gate_count[1]));
DRIVER V3 (.A(pp_w[9]), .Z(pp1_W[12]), .number(gate_count[2]));
DRIVER V4 (.A(pp_w[9]), .Z(pp1_W[13]), .number(gate_count[3]));
```

We will rank all students according to $A \cdot T$, where A represents the **number of transistors** and T represents the **total execution time**.

Your approximation error score and performance score will be graded by your ranking according to the table below, respectively.

Percentage of students	Approx. Error Score	Performance Score
If your ranking is > 90 %	35	35
80% ~ 90%	32	32
70% ~ 80%	28	28
60% ~ 70%	25	25
50% ~ 60%	21	21
40% ~ 50%	18	18
30% ~ 40%	14	14
20% ~ 30%	11	11
10% ~ 20%	7	7
0% ~ 10%	4	4
Not using standard cell logic	0	0
Plagiarism	0	0
Incorrect number connection	0	0

2. Report (30%)

(a) Simulation (0%)

Specify your **minimum cycle time**. **If you do not provide this information, You will not get any score for part 1 (70%)". This minimum cycle time would be verified by TAs.** Also, please put the screenshot of the summary provided by the testbench in the report.

(b) Circuit diagram (10%)

You are encouraged to use software to draw the architecture **instead of hand drawing**. Plot it **hierarchically** so that readers can understand your design easily. **All of the above will improve your report score.**

(5%) Plot the gate-level circuit diagram of your design.

(5%) Plot the critical path on the diagram above.

(c) Discussion (20%)

Discuss your design.

➤ (5%) Introduce your design.

➤ (5%) How do you improve your critical path and the number of transistors?

- (5%) How do you trade-off between area and speed?
- (5%) Compare with other architectures you have designed (if any).

Notification


Following are the files HW4.zip includes

- **HW4_2023.pdf:** This document.
- **HW4_tutorial_2023.pdf:** Tutorial in class.
- **sigmoid.v:**
Dummy design file. Program the design in this file.
The header of the top module and the declaration of the I/O ports are predefined in this file and you are not allowed to change them.
- **lib.v:**
Standard cells.
- **tb.v:**
The testbench for your design.
- **pattern/Inn.dat:**
Input patterns for the testbench. Please keep the hierarchy when simulation.
- **pattern/Gol.dat:**
Patterns of the real hyperbolic tangent values for the testbench. Please keep the hierarchy when simulation.

Submission

All students who do not submit files according to the rules **will get a 20% penalty.**

 - You should upload a **zip file** to **NTUCool**, the file name is “HW4_Student ID”, e.g., HW4_b10901001.zip
- Your file must conform to the following structure.



- Specify your cycle time in CYCLE.txt, e.g.,



Testbench

1. Description

- The output waveform will be dumped to file "sigmoid.fsdb", you can use nWave to examine it.
- You can change the number of test data to debug, but the final error will still test 256 data. (**define PATTERN 256**)
- You can enable the debug function, which will display the data received.

```

Pattern 128. / Output: 16384 / Golden: 16384 / MSE: 0
Pattern 129. / Output: 16896 / Golden: 16639 / MSE: 258
Pattern 130. / Output: 17408 / Golden: 16895 / MSE: 1028
Pattern 131. / Output: 17920 / Golden: 17151 / MSE: 2310
Pattern 132. / Output: 18432 / Golden: 17406 / MSE: 4112
Pattern 133. / Output: 18944 / Golden: 17661 / MSE: 6430
Pattern 134. / Output: 19456 / Golden: 17915 / MSE: 9276
Pattern 135. / Output: 19968 / Golden: 18168 / MSE: 12656
Pattern 136. / Output: 20480 / Golden: 18421 / MSE: 16560
Pattern 137. / Output: 20992 / Golden: 18672 / MSE: 21025
Pattern 138. / Output: 21504 / Golden: 18923 / MSE: 26021
Pattern 139. / Output: 22016 / Golden: 19172 / MSE: 31595
Pattern 140. / Output: 22528 / Golden: 19420 / MSE: 37733

```

Note that the testbench discards the least 16 bits of the error in order to shrink the its length.

- If you pass the simulation, you should see:

```

=====
Simulation finished
=====

```

You will also see the summary:

```

=====
Summary
=====
Clock cycle:          10.0 ns
Number of transistors: 1061
Total excution cycle: 256
Approximation Error Score: 17987801.0
Performance Score:    2716160.0
=====

```

2. Simulation Command

```
> vcs tb.v sigmoid.v lib.v -full64 -R -debug_access+all +v2k
```

```
> vcs tb.v sigmoid.v lib.v -full64 -R -debug_access+all +v2k +define+DEBUG
```

If you have any questions or problems with this homework, feel free to contact TA.

TA: 陳丕全 Email: r11943013@ntu.edu.tw, EE2-329

HW4 Office hours: 12/12 Tue 14:00~16:00 @EE2-329

12/13 Wed 14:00~16:00 @EE2-329

If you are not available during office hours, you can email the TA to make an alternative appointment.